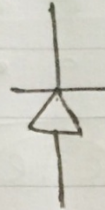




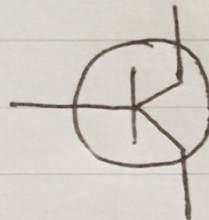
## Diode


\* N type material + P type material  
= Diode




\* N type material + P type material  
+ N type material = transistor



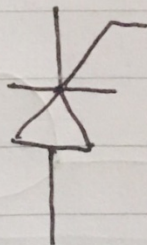
\* N type material + P type material  
+ N type      u      + P u u  
= thyristor



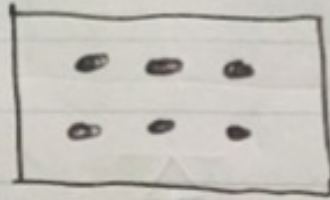\* N type material ৩০-মার্চ-  
অনেক free ইলেকট্রন রয়েছে





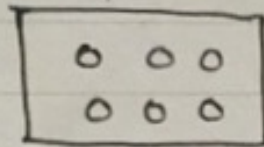\* P type material ৩০-মার্চ-  
অনেক free hole রয়েছে




↓  
movement of  
electron

Connection

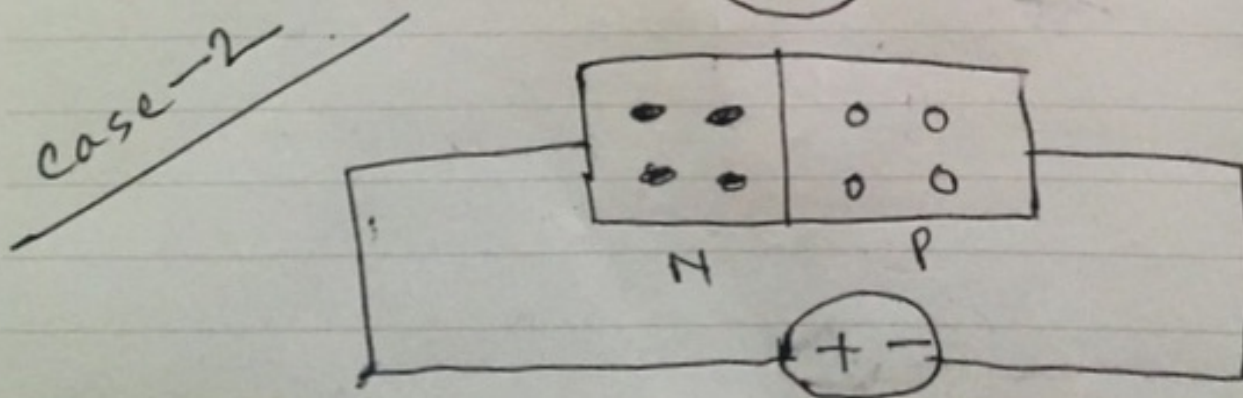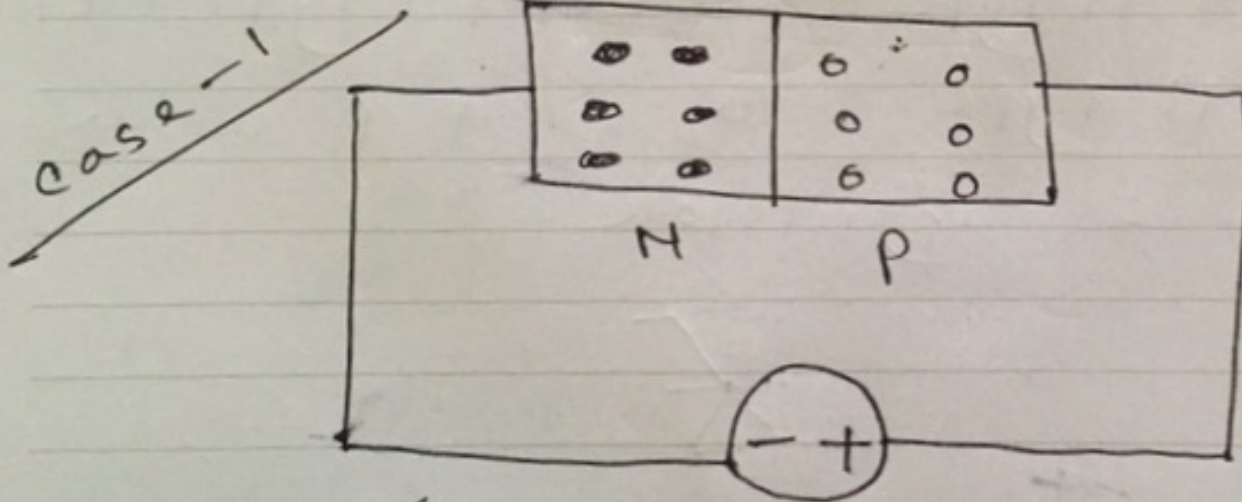




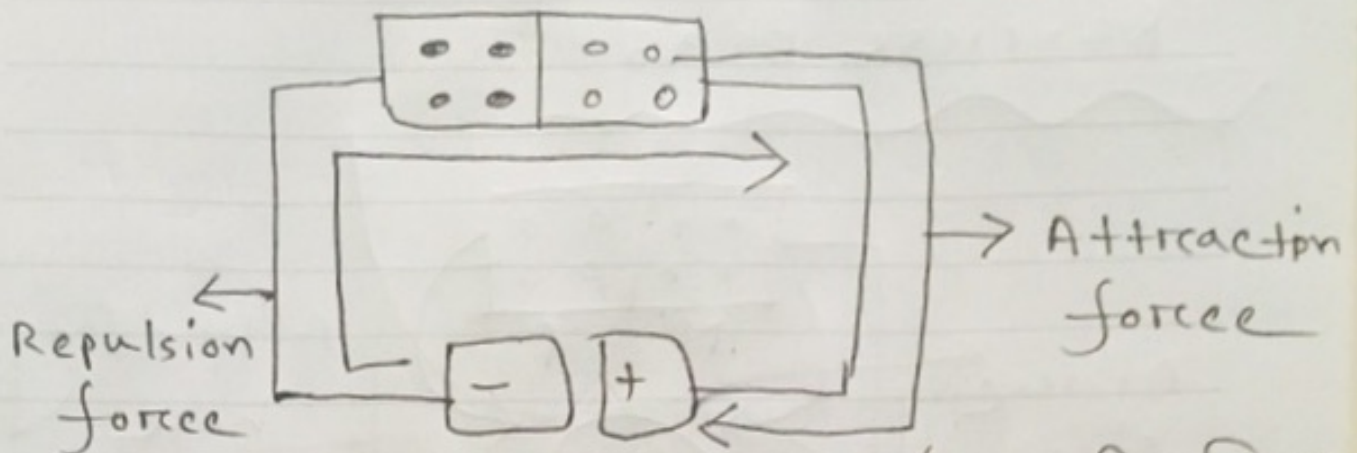

Source (or) positive terminal  
 → Repulsion force  
 → Attraction force  
 → Source (or) negative terminal  
 → Attraction force

## Diode circuit (forward Bias)

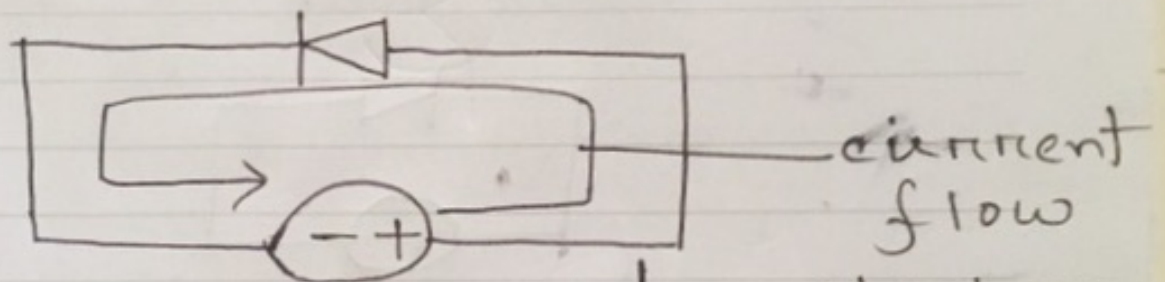


current flow  
 electron flow (or)  
 direction


→ Diode (or) p-type  
 source (or) positive  
 terminal, N-type  
 source (or) negative  
 terminal connect to  
 source (or) negative terminal  
 current pass through circuit  
 (or) direction



## Reverse Bias

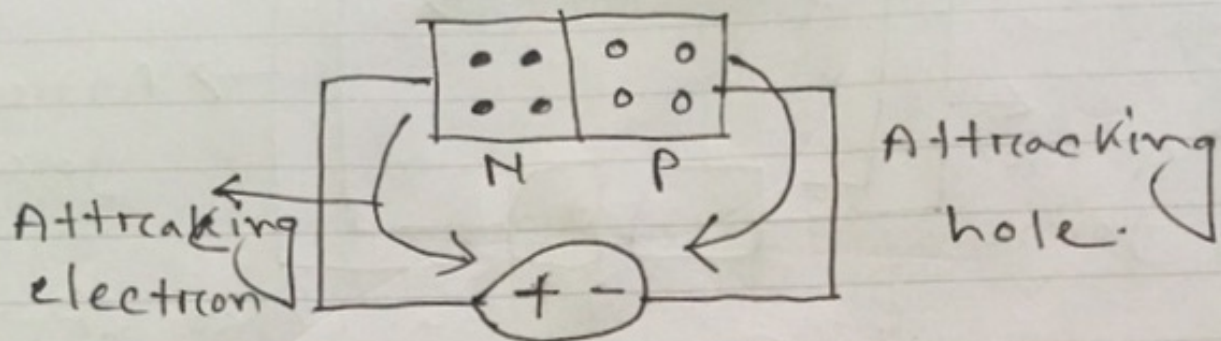

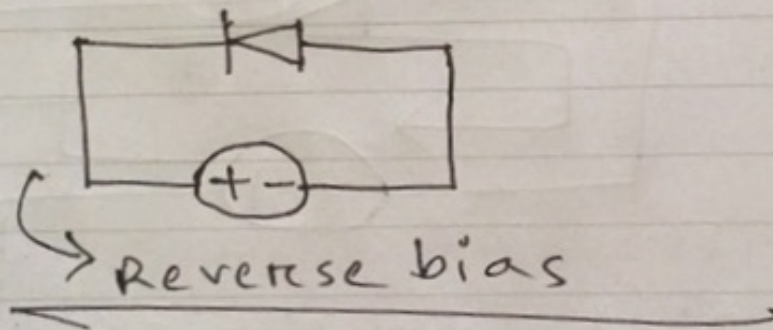Reverse Bias  $\rightarrow$  current flow  $\nrightarrow$   $\nrightarrow$



Diode  $\rightarrow$  P type  $\rightarrow$

Negative  $\rightarrow$  connect  $\rightarrow$  N type  $\rightarrow$

positive  $\rightarrow$  connect  $\rightarrow$  Diodes current  $\rightarrow$



flow 2(3) पा(0) ना मा(0) Reverse  
bias — 0(न)।

## Characteristics Curve

Q If there is only characteristics curve


Current-voltage curve of electrical device or component is a graphical curve which is used to define its operation within electrical circuit.

If there is more than one characteristics curve

Current-voltage curve of electrical device or component is a ~~geo~~ group of graphical curve which is used to define its operation within electrical circuit.



## Curve

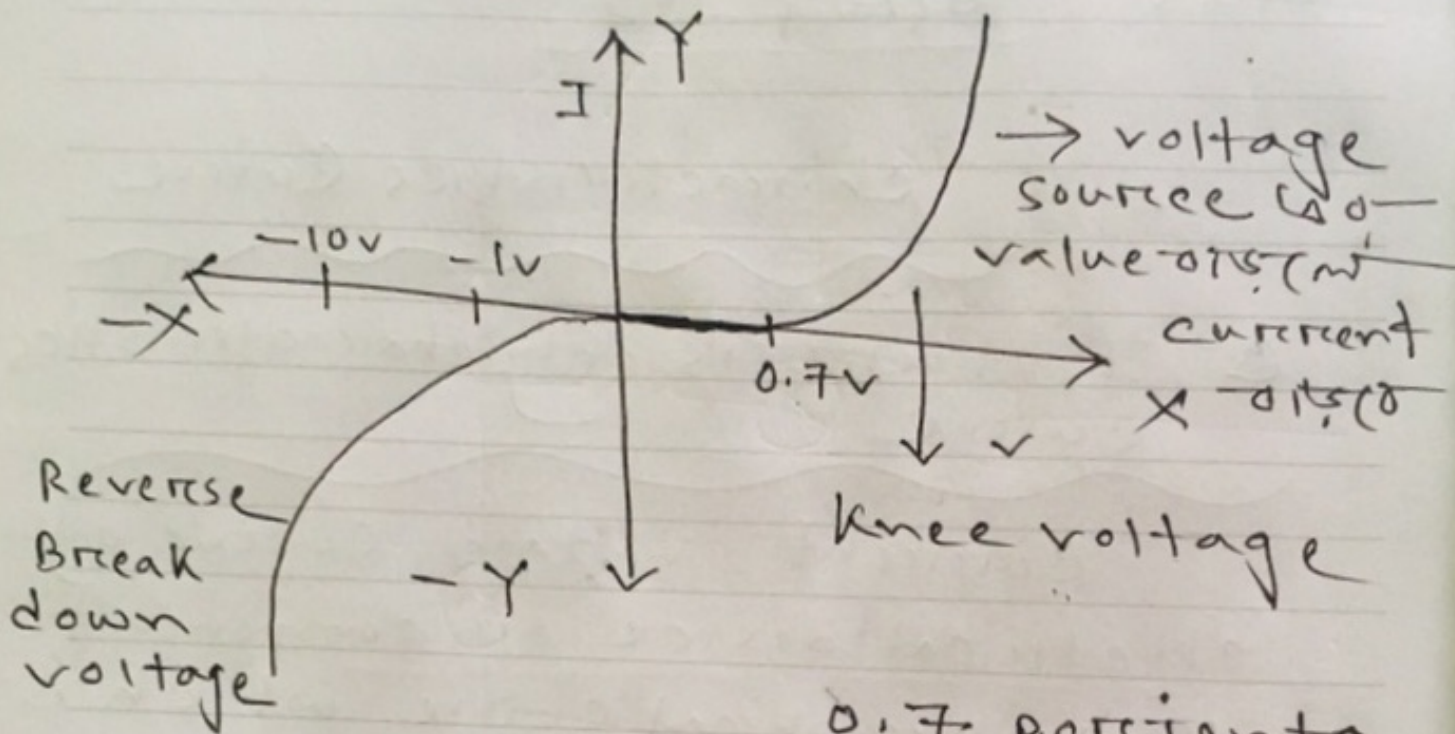

0.7 portion to  
current 0 A





## Linear circuit


$$y = ax$$

$x$  = input

$y$  = output

$a$  = constant

$I = aV$ , + the circuit is linear

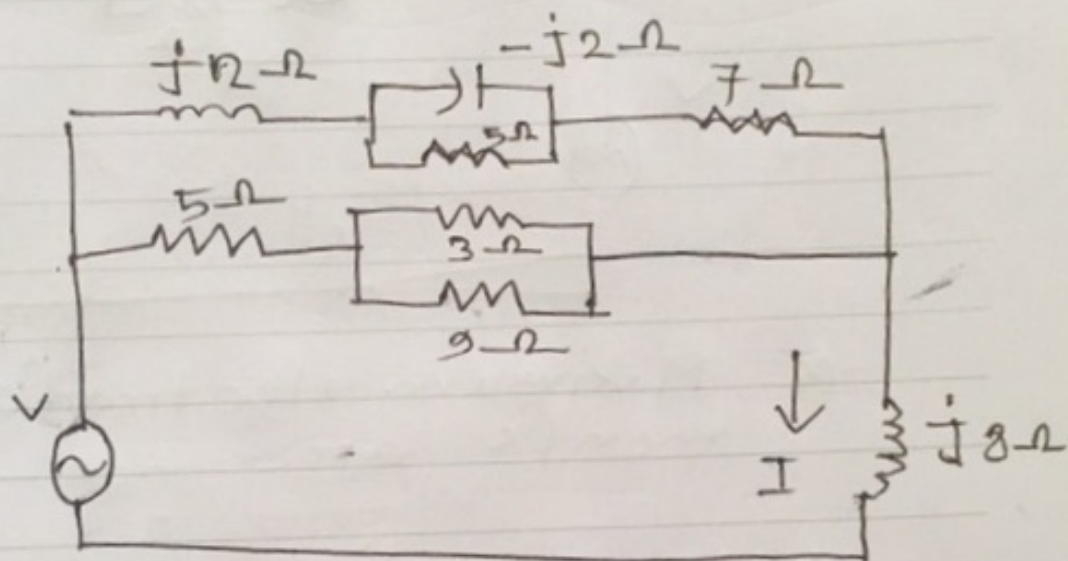


★ Generally, basic electrical circuits are linear,

★ In linear circuits, Ohm's law, Nodal analysis, Mesh analysis, superposition theorem etc are applicable

## Non linear Circuit

$$y \neq ax$$

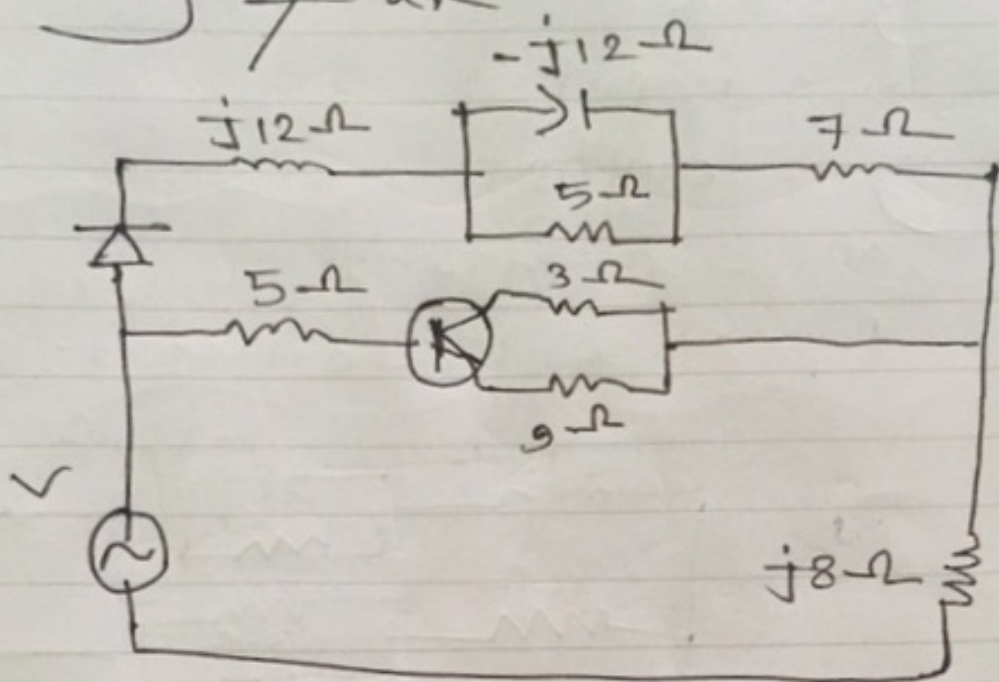

→ Maximum electronic equipments are non-linear.


→ In non-linear circuit, Ohm's law, Nodal analysis, Mesh analysis, Superposition theorem etc are not applicable.


→ That's why we need Equivalent circuit.






## 3 types diode equivalent circuit

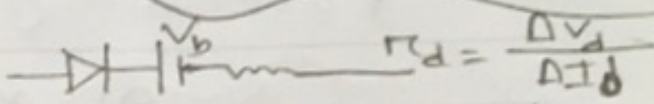1) ~~Approximate~~   $r_d = \frac{\Delta V_d}{\Delta I_D}$   
Approximate or piecewise  
Linear equivalent circuit

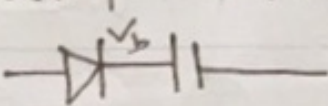2) simplified equivalent circuit  
or constant voltage drop  
model   $r_d = 0 = \frac{1}{g_d}$   
 $g_d = \infty = \infty$

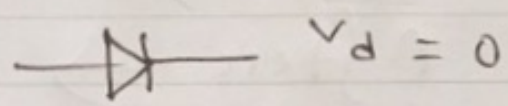3) Ideal equivalent circuit.  
  $V_d = 0$


→ Diode  $\hookrightarrow$  P type  $\hookrightarrow$   
 $\hookrightarrow$   $\hookrightarrow$  voltage source  
 $\hookrightarrow$  positive, N type  
 $\hookrightarrow$   $\hookrightarrow$  voltage source  
 $\hookrightarrow$  Negative.

$$V_{\text{source}} = V_b \quad (b = \text{built-in potential})$$


for Si,  $V_b = 0.7\text{ V}$

for a circuit having  
a diode

before  $\rightarrow$

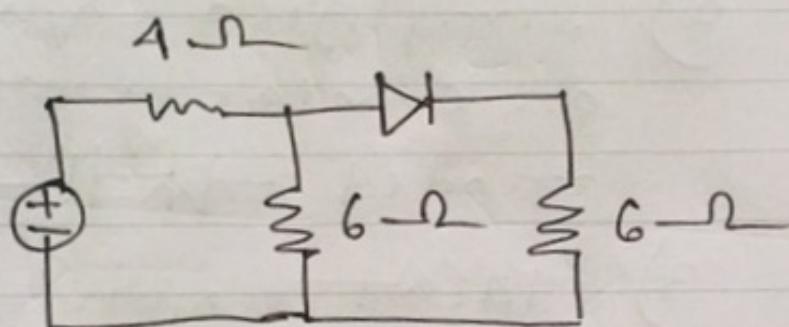

After  $\rightarrow$


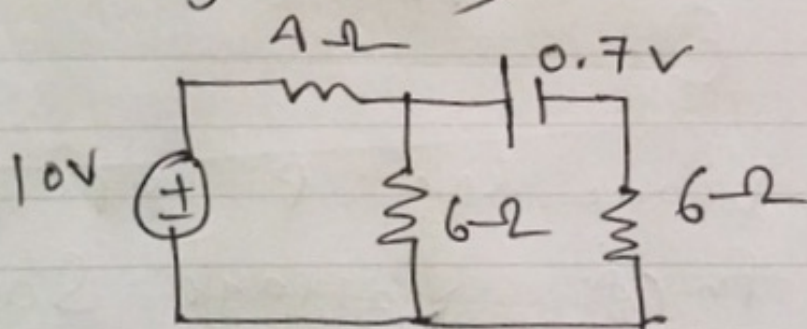






## Example

Determine current  $I$  from the circuit

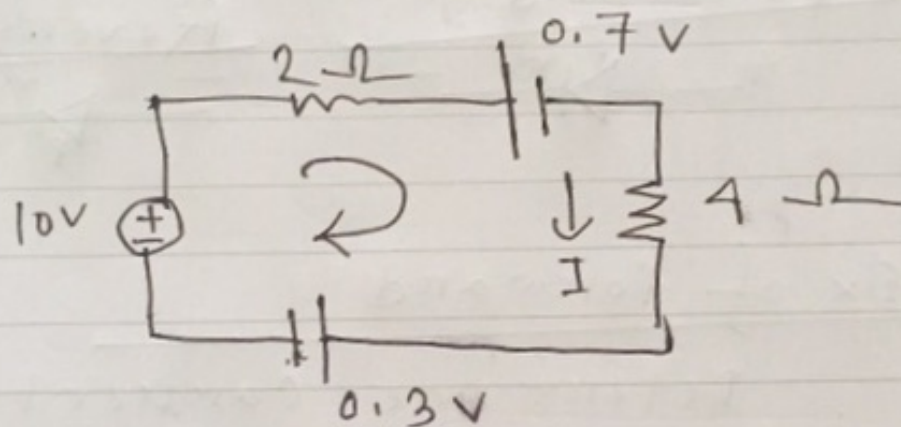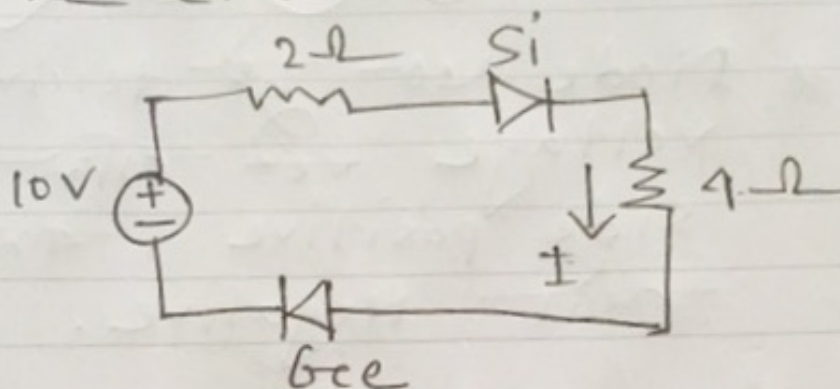

$$-10 + 2I + 0.7 + 4I + 0.3 = 0$$

$$\underline{\underline{I}}$$



$$\Rightarrow 6I = 10 - 0.7 - 0.3$$

$$\Rightarrow I = \frac{9}{6} A$$

$$= 1.5 A$$



How to understand biased condition  
(Forward or Reverse)?

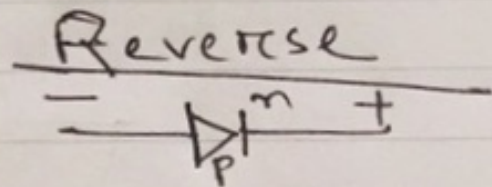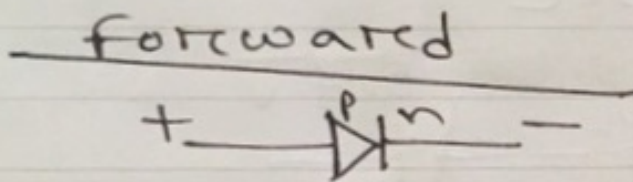\* Diode ko  $\frac{P}{N}$  terminal ko  
voltage  $\frac{P}{N}$  side positive,  $\frac{N}{P}$  side  
negative.



Ex of forward

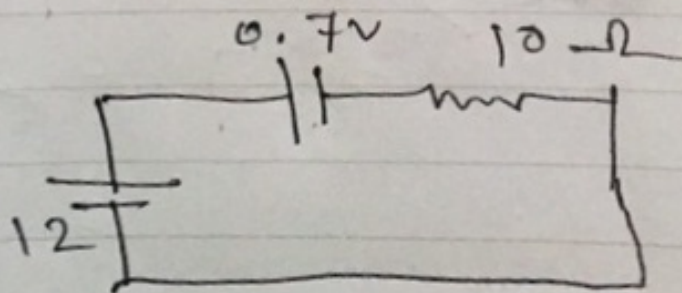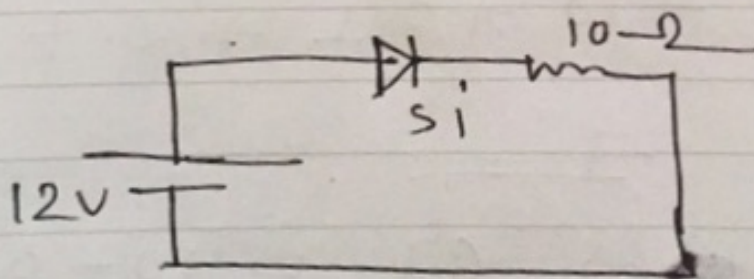
Determine current through  
10 ohm resistor.









$$(12 - 0.7) = 11.3 \text{ V}$$

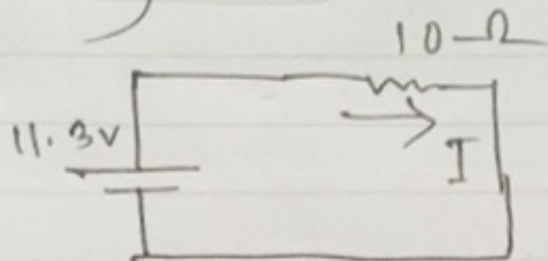

$$I = \frac{11.3}{10} = 1.13 \text{ A}$$

For Reverse

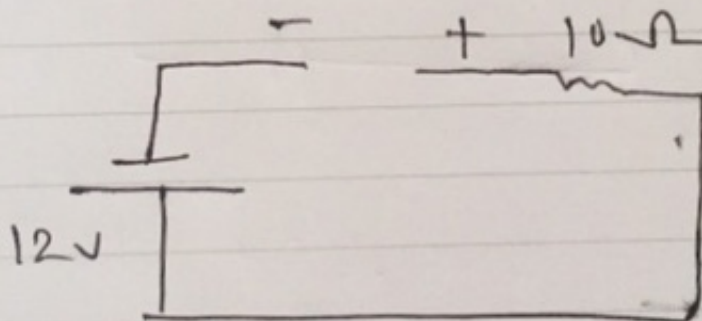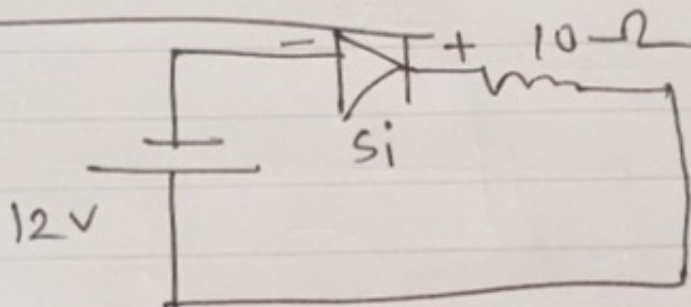

$$I = 0 \text{ (bez of reverse bi)}$$