

Operational Amplifier

Symbols


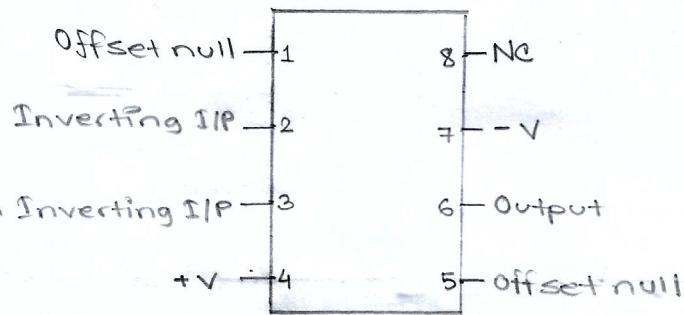
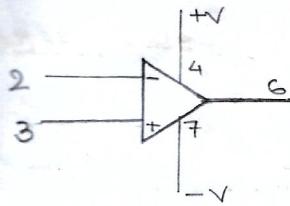
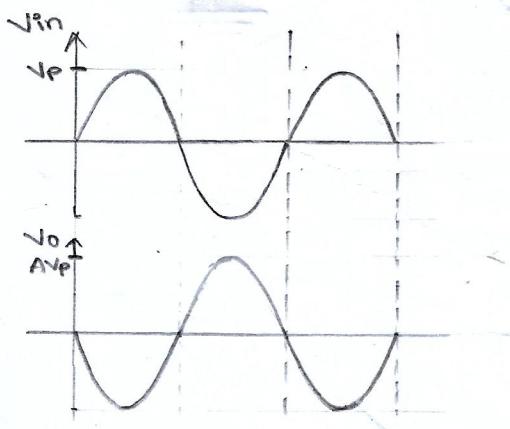


Fig : Pin configuration

Inverting Operation of OP-Amp's


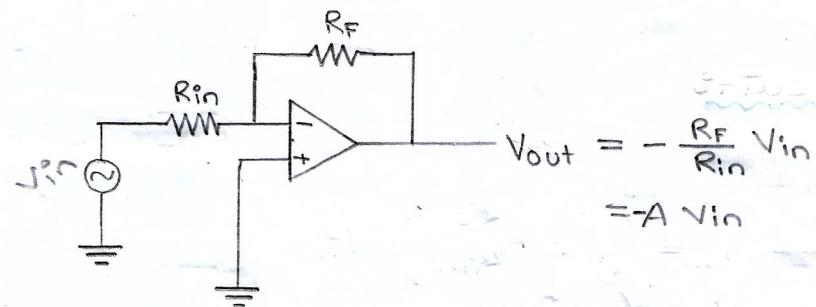


$$V_{out} = -\frac{R_F}{R_{in}} V_{in}$$




$$= -A V_{in}$$

Op-Amp Applications

Non-Inverting Operation of Op-Amp:

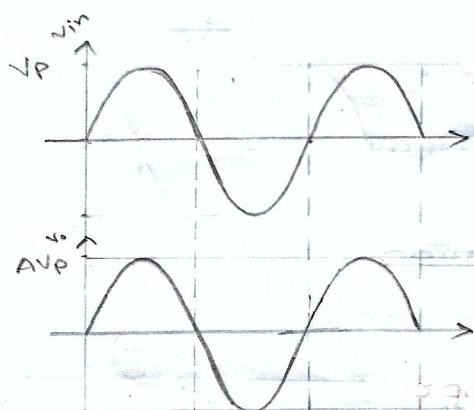
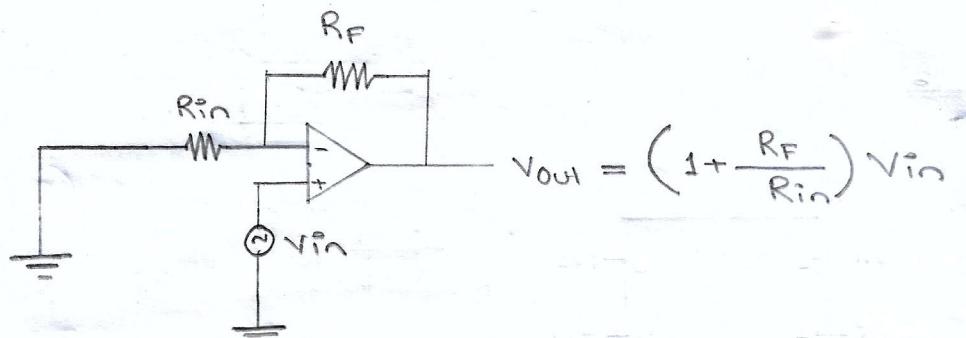


Voltage follower Circuits

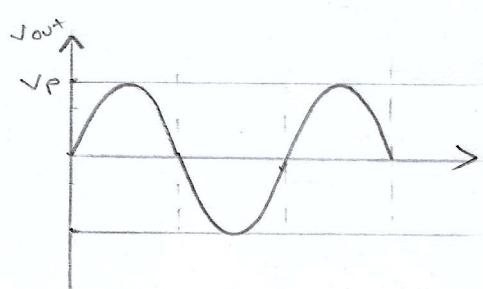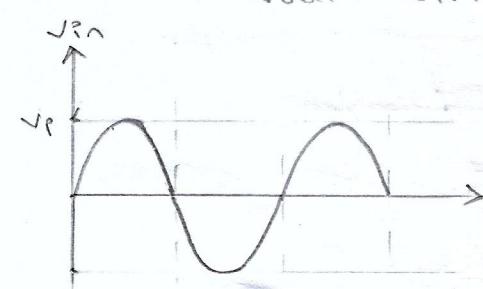
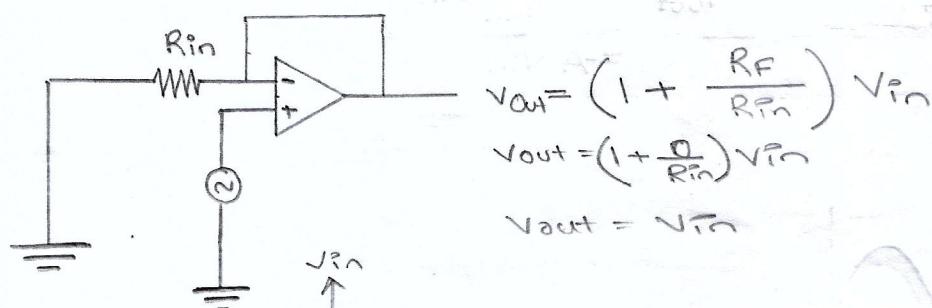


Comparator Circuits



DC \rightarrow P-N°

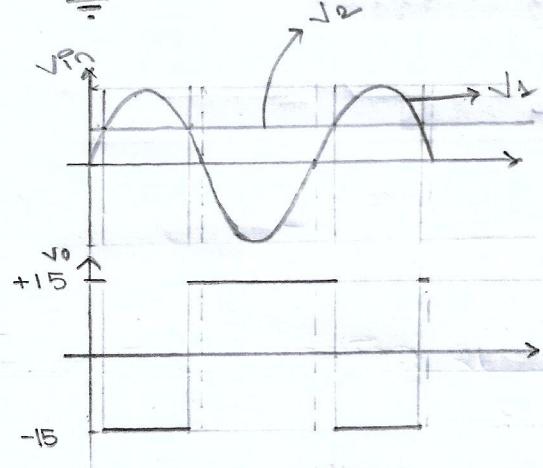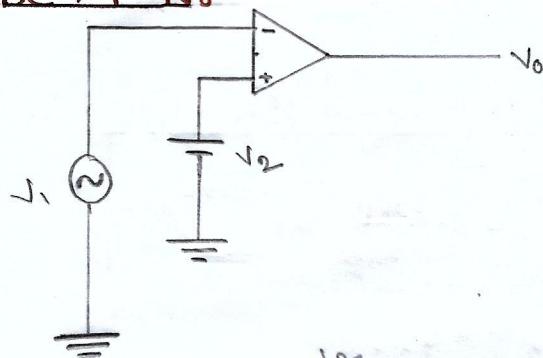

DC \rightarrow N-P°

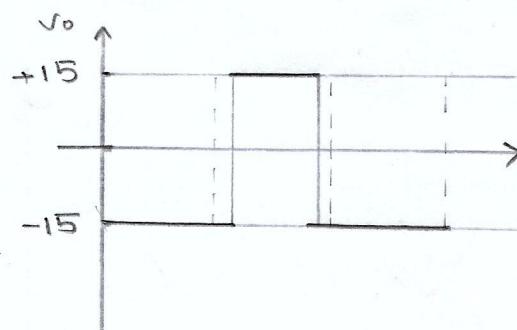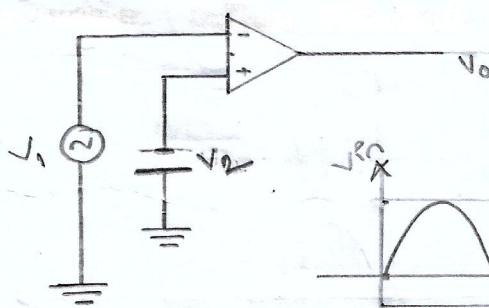

Zero - Crossing Detector

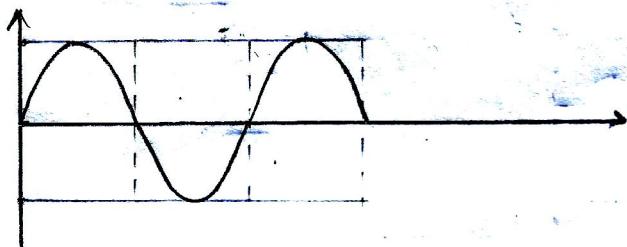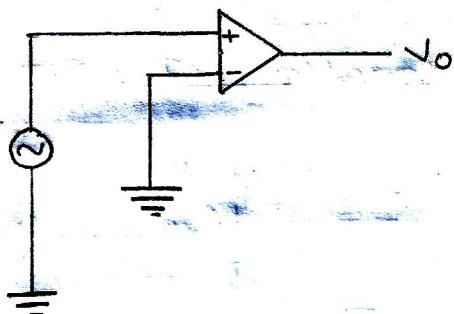


DG \leftrightarrow N-6



Positive

Half wave Rectifier

Forward Bias Diode

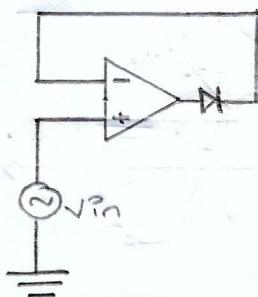

AC

DC

AC



DC

$$V_o = \left(1 + \frac{R_f}{R_{in}}\right) V_{in} \Rightarrow V_{out} = V_{in}$$

OS

Forward Bias Diode

Forward DC Voltage

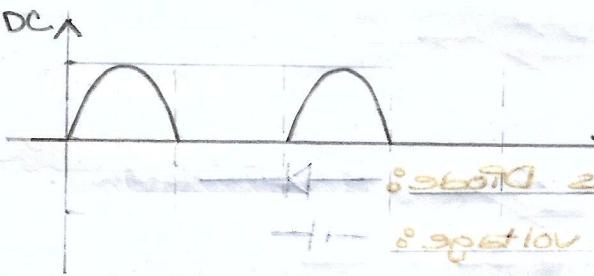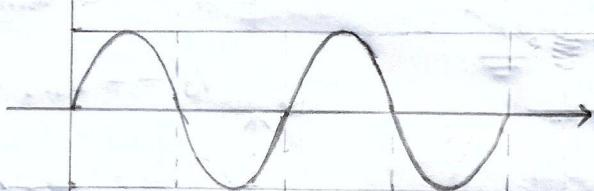


Negative DC voltage

Forward Bias Diode

Negative

Halfwave Rectifier

Reverse Bias Diode


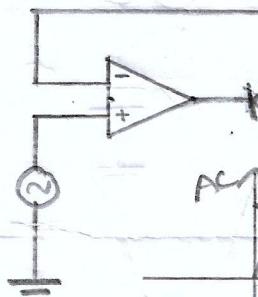


AC

DC

AC



DC

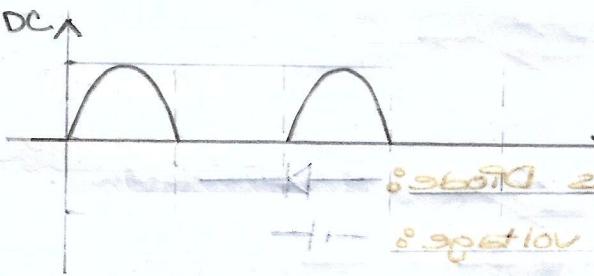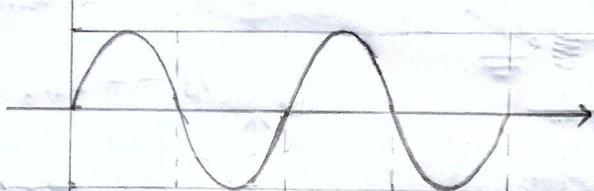

Clipper's Circuits



Forward Bias Diode: \rightarrow

Positive DC voltage: \rightarrow

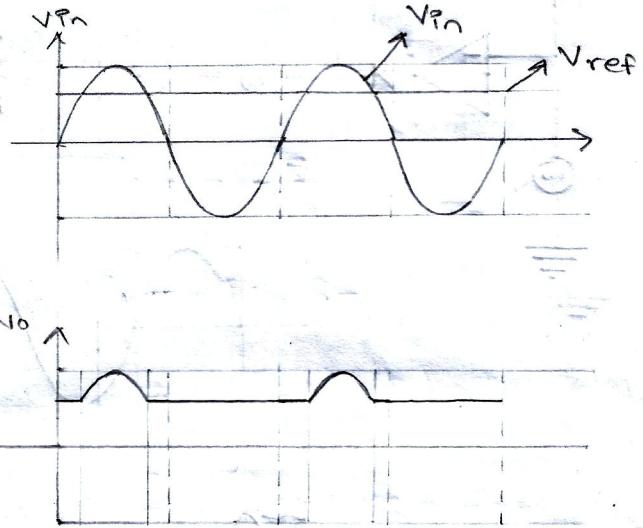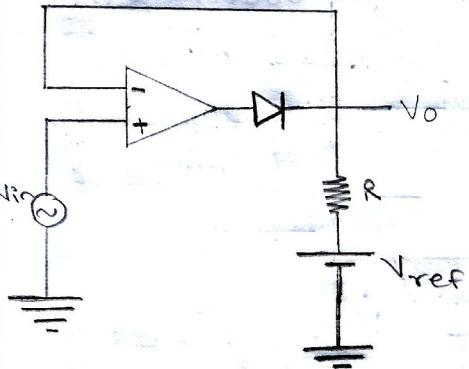



Forward Bias Diode: \rightarrow

Negative DC voltage: \rightarrow

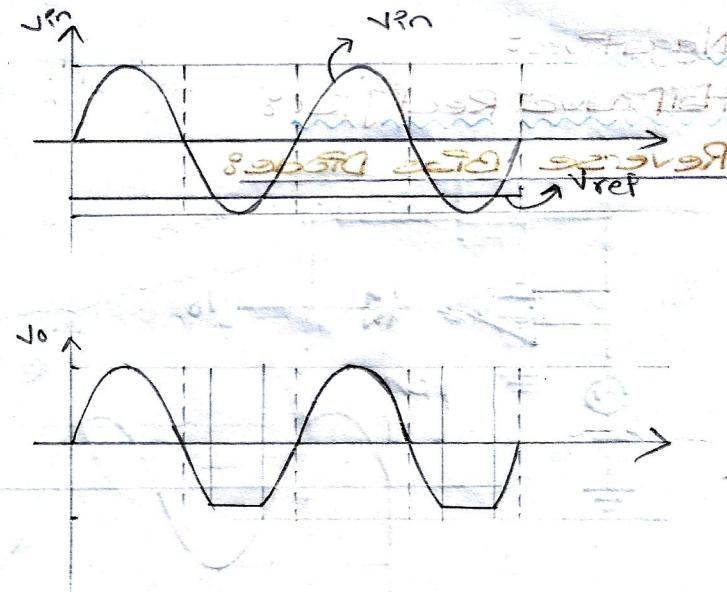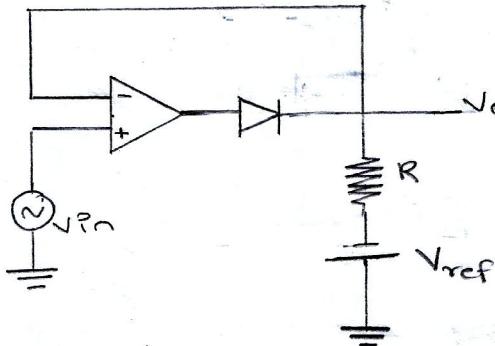



Reverse Bias Diodes \leftrightarrow

Positive DC voltage: \rightarrow

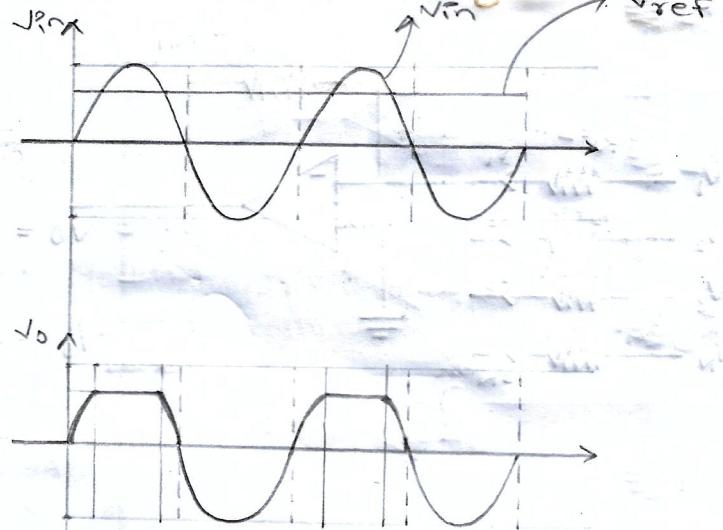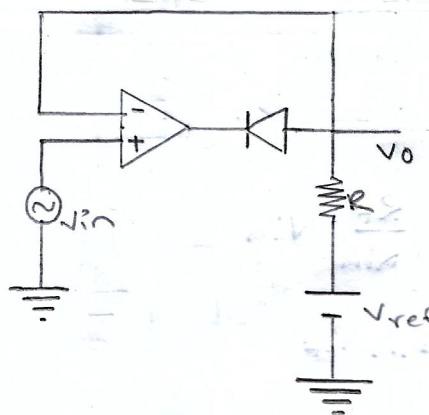


Reverse Bias Diodes \leftrightarrow

Negative DC voltage: \rightarrow

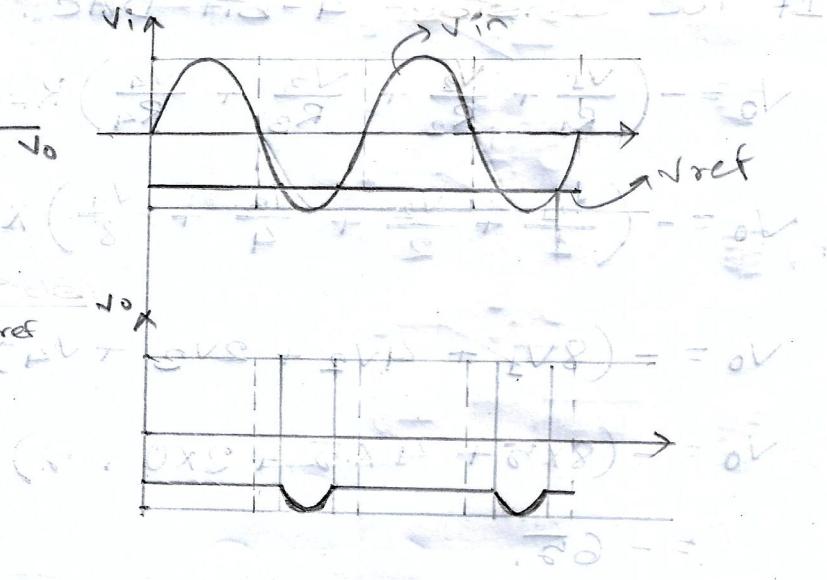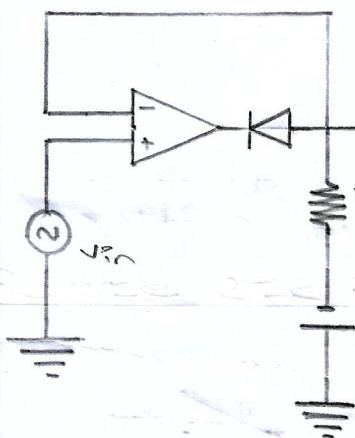

Digital to Analog Converter (DAC) section 2

Binary Weighted DAC

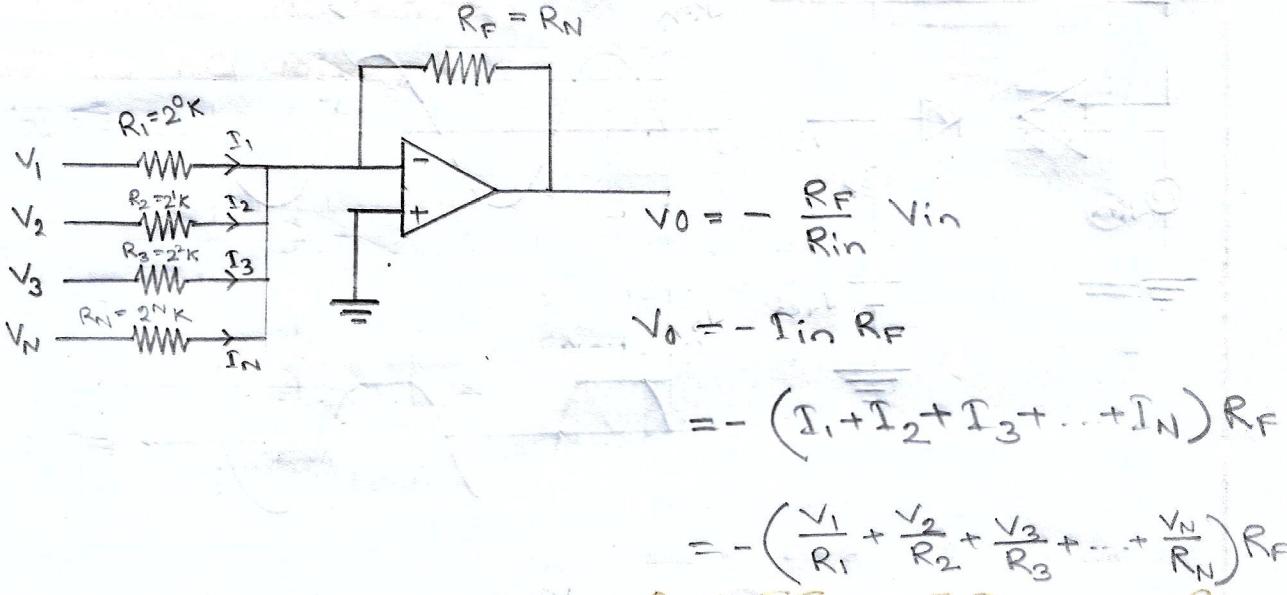

If we consider 4-bit DAC.

$$V_0 = - \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right) R_F$$

$$V_0 = - \left(\frac{V_1}{1} + \frac{V_2}{2} + \frac{V_3}{4} + \frac{V_4}{8} \right) \times 8.$$

$$V_0 = - (8V_1 + 4V_2 + 2V_3 + V_4)$$

$$V_0 = - (8 \times 5 + 4 \times 5 + 2 \times 0 + 5)$$


$$= - 65.$$

ADC:

:50A 50-5

2 bit ADC:

$V_{ref} = 8V$

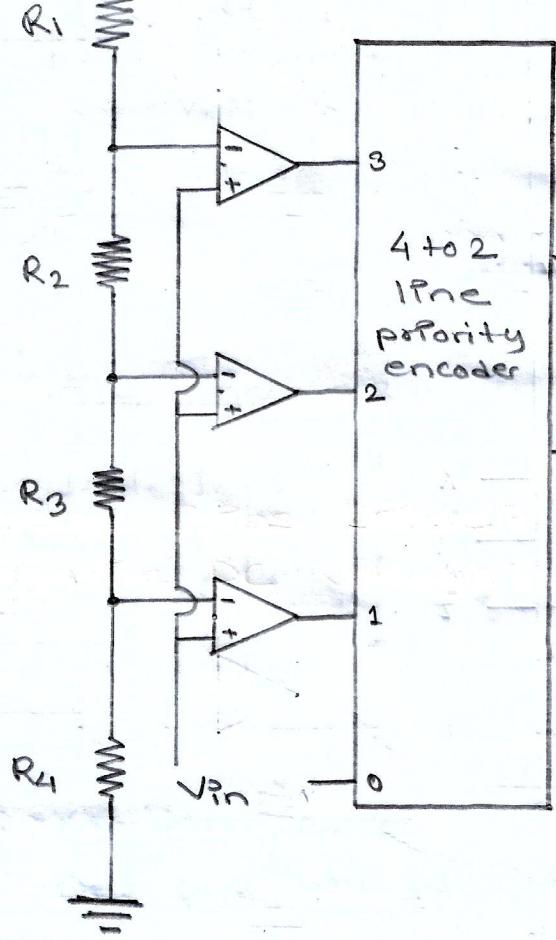


$$OP = 2^2 - 1 \\ = 3$$

$$R = 2^2 = 4.$$

$$\sin \theta = 1 - \cos^2 \theta = 90$$


$$\theta = 90^\circ = 9$$

3-bit ADC

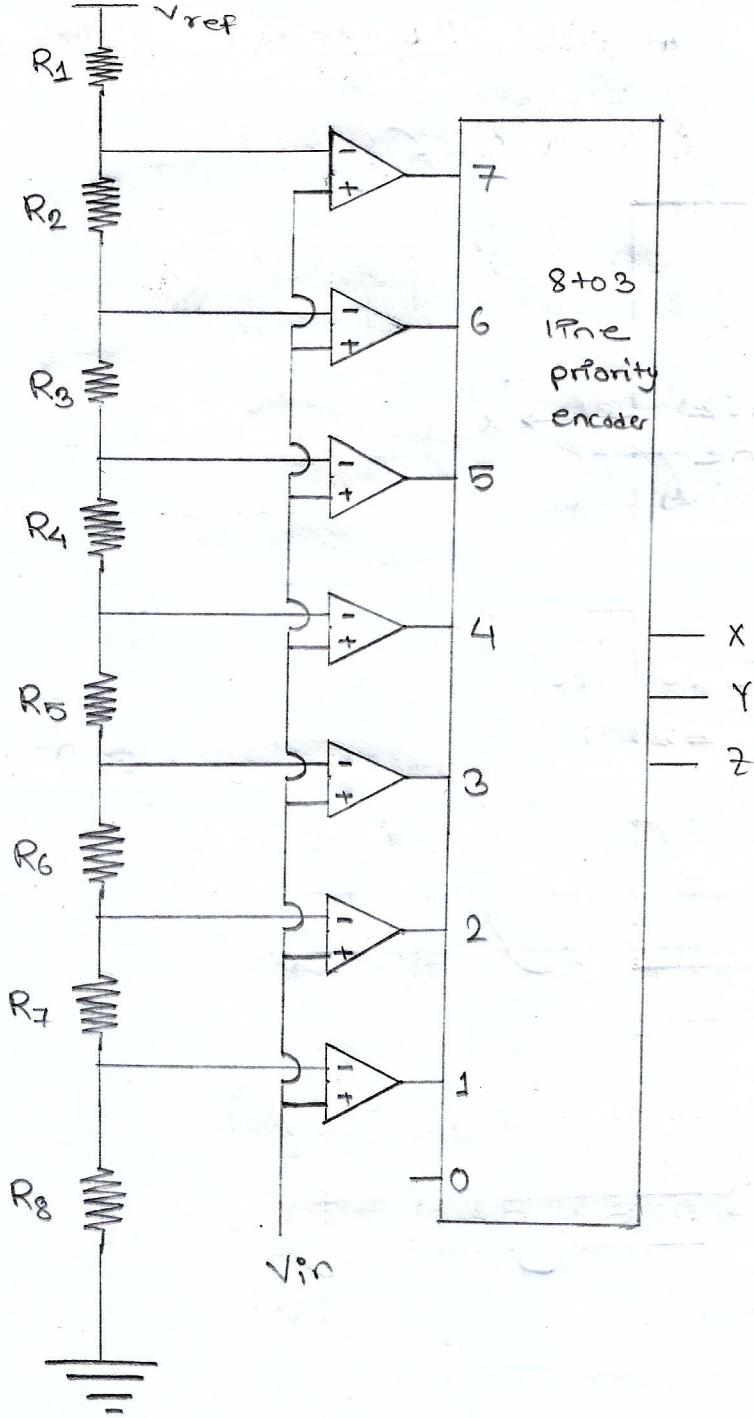

$$OP = 2^3 - 1 = 7.$$

$$R = 2^3 = 8.$$

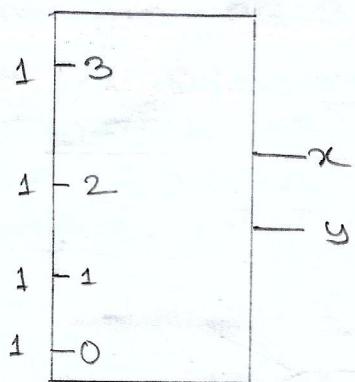

I_0	I_1	I_2	I_3	x	y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$x = \bar{I}_0 \bar{I}_1 I_2 \bar{I}_3 + \bar{I}_0 \bar{I}_1 \bar{I}_2 I_3$$

Priority encoders

I_0	I_1	I_2	I_3	x	y
X	X	X	1	1	1
X	X	1	0	1	0
X	1	0	0	0	1
1	0	0	0	0	0

I_3 High priority.

I_2

I_1

I_0 Low priority

Note:

X = Dont care

Output will always depend on the priority list.

Successive Approximation ADC


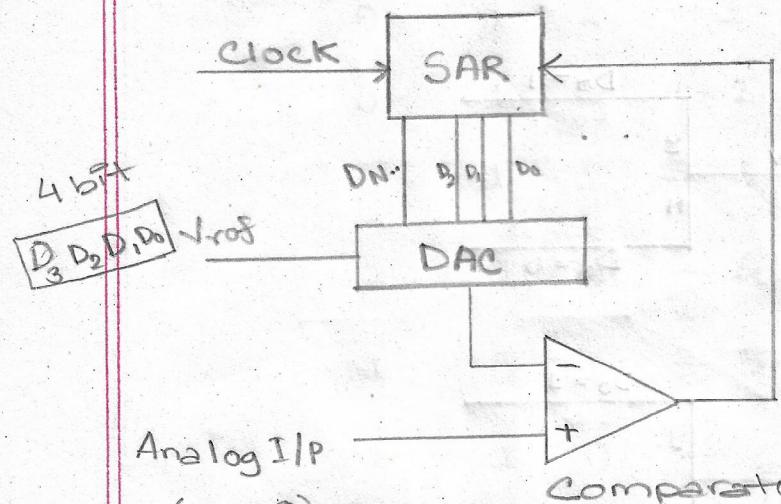


Fig: Block diagram of a SA ADC.

SA ADC for next slide cont

$$* 2 - 3v = 2 \text{ bits} \quad (4) \vee \quad * 15 - 16v = 4 \text{ bits} \quad (16) \vee$$
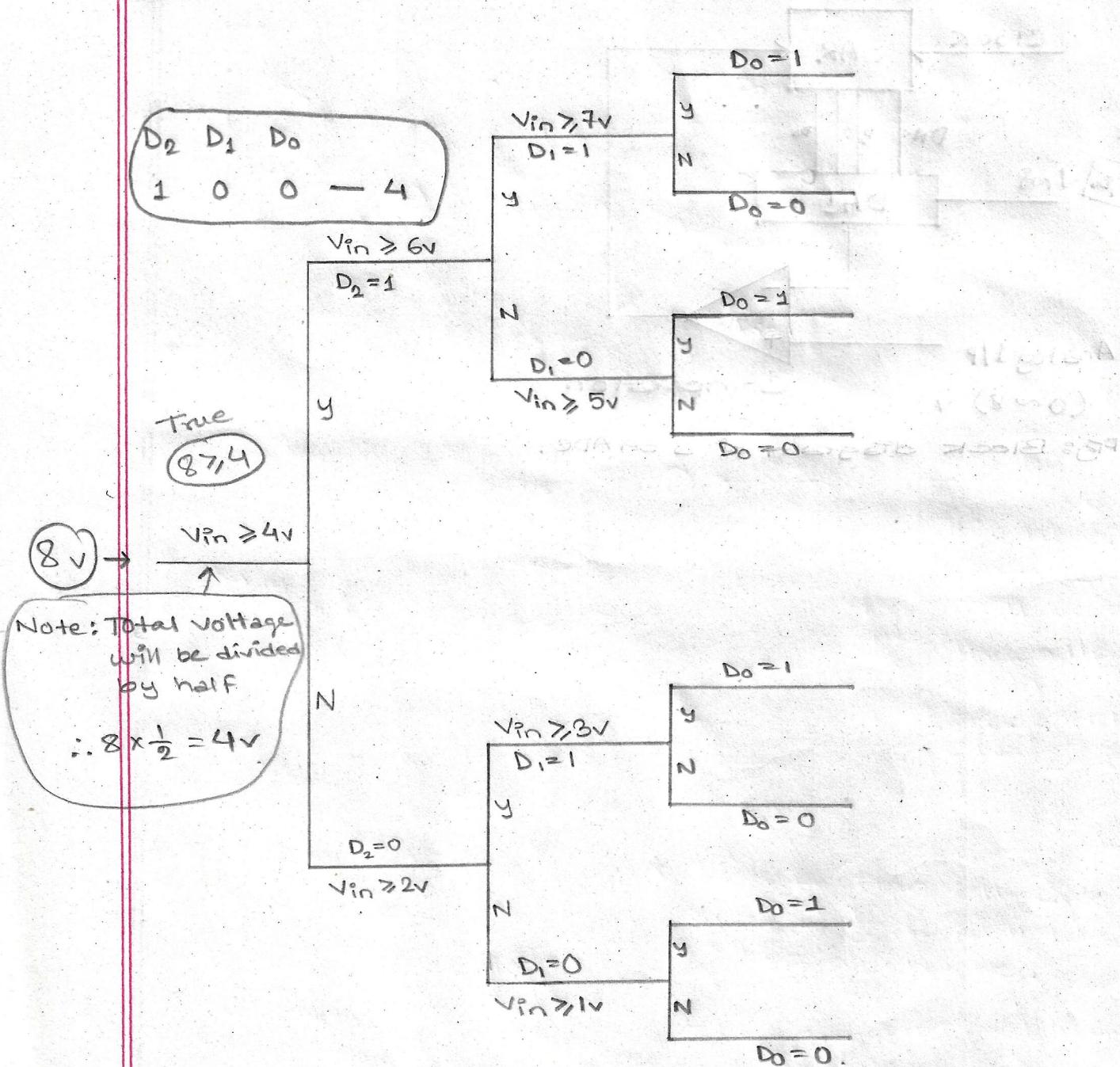
$$* 4 - 5v = 3 \text{ bits} \quad (8) \vee \quad * 30 - 32v = 2 \text{ bits} \quad (32) \vee$$



Tree diagram of SA ADC

Note^o D₂ D₁ D₀

0 0 0 - 0

0 0 1 - 1

0 1 0 - 2

0 1 1 - 3

1 0 0 - 4

1 0 1 - 5

1 1 0 - 6

1 1 1 - 7.

∴ we can convert
voltage into bit.

∴ If V_{in} = 4.75V = 1 0 0.

Q. Find out Binary bit for an input voltage of
3.9V using SA ADC.

555 Timers



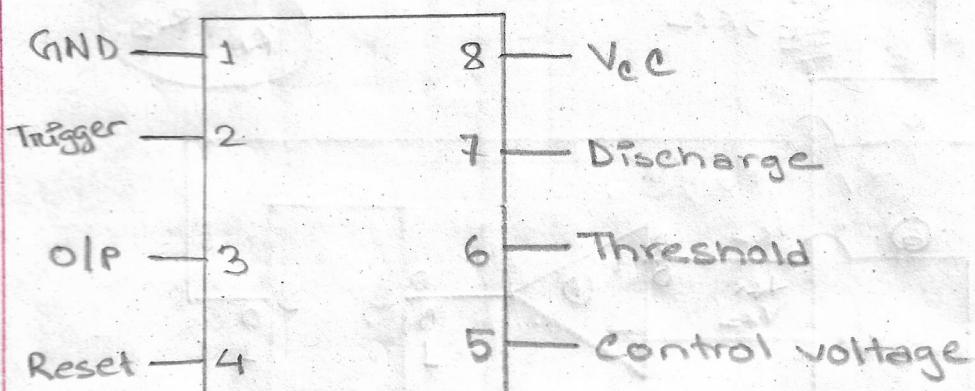


Fig: Pin Configuration

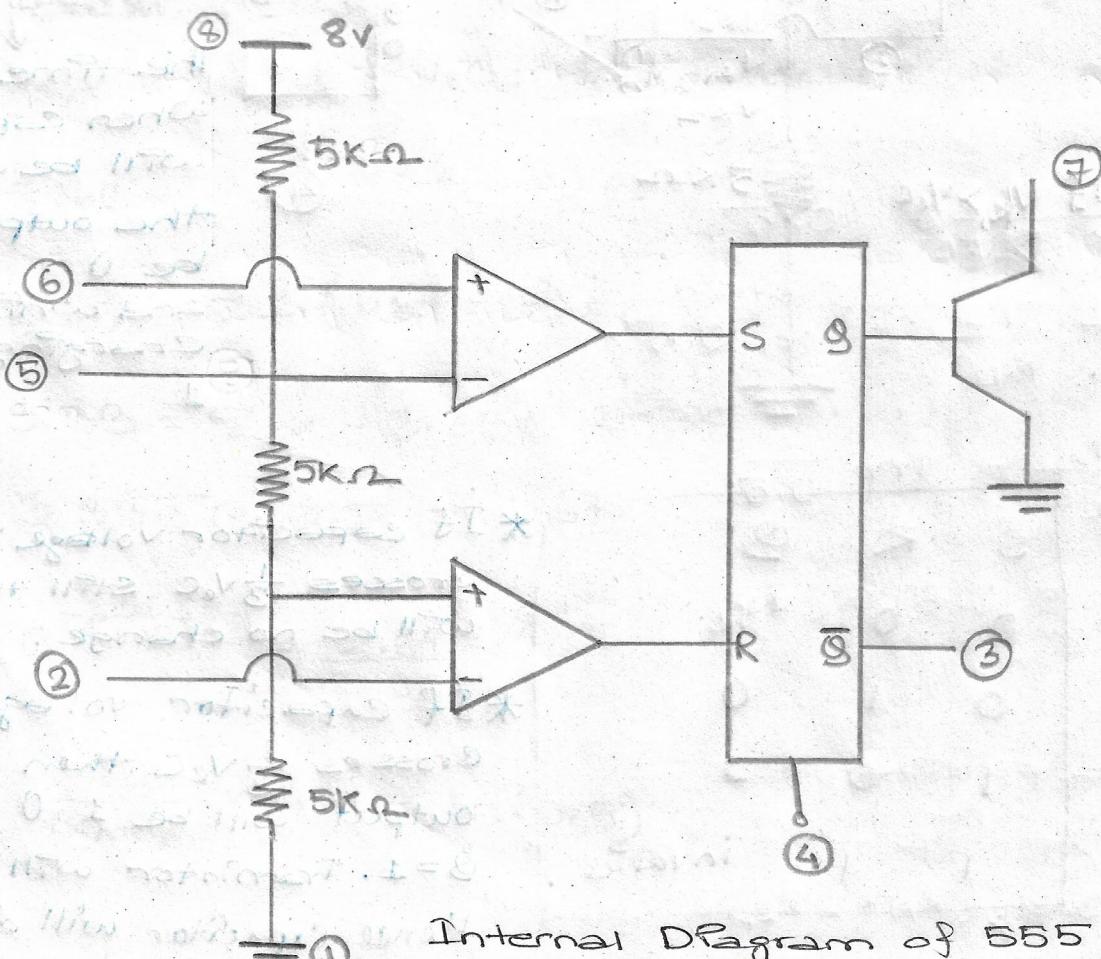

Internal Diagram of 555 Timer.

Astable Operation of 555 Timer:

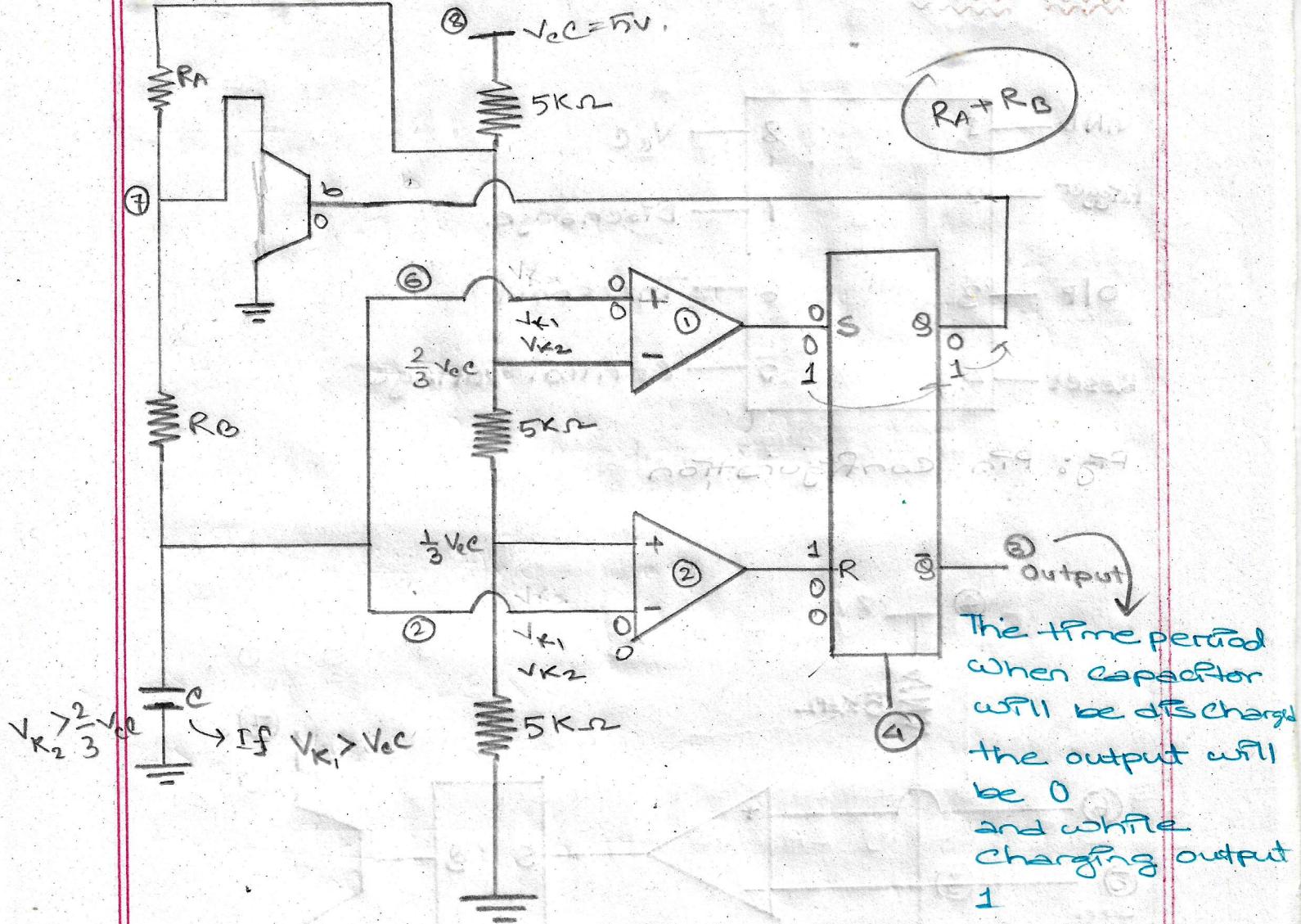


The time period when capacitor will be discharged the output will be 0 and while charging output

Note:

S	R	G	
0	0	N/c	
0	1	0	
-	0	1	
1	1		invalid

* If capacitor voltage V_K crosses $\frac{1}{3}V_{cC}$ still there will be no change.

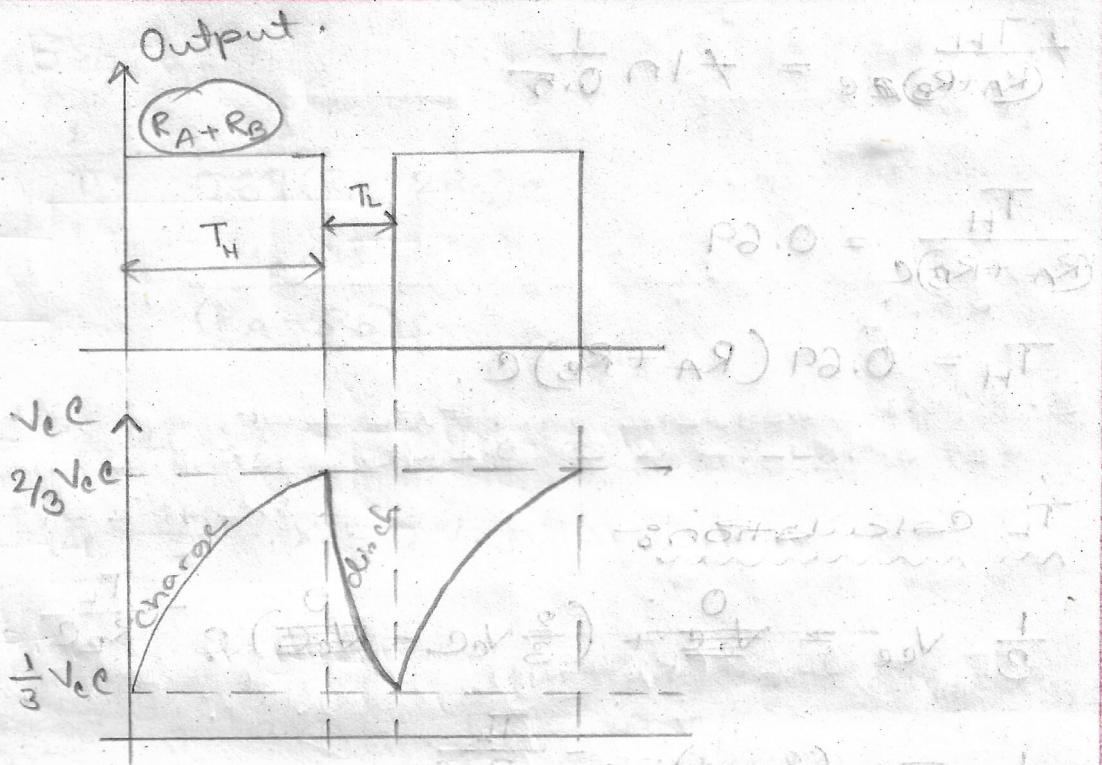* If capacitor voltage V_{C2} crosses $\frac{2}{3} V_{el}$ then output will be 1, 0 so $S = 1$. Transistor will short. Hence capacitor will discharge until it gets lower than $\frac{1}{3} V_{el}$



TH Calculation:

$$V_{out} = V_{cc} + \left(\frac{1}{3} V_{cc} - V_{cc} \right) e^{-\frac{T_H}{(R_A+R_B)C}}$$

$$\frac{2}{3} V_{cc} = 5 + \left(\frac{1}{3} \times 5 - 5 \right) e^{-\frac{T_H}{(R_A+R_B)C}}$$

$$\frac{2}{3} \times 5 = 5 + (1.67 - 5) e^{-\frac{T_H}{(R_A+R_B)C}}$$

$$3.33 = 5 - 3.33 e^{-\frac{T_H}{(R_A+R_B)C}}$$

$$3.33 e^{-\frac{T_H}{(R_A+R_B)C}} = 1.67$$

$$e^{-\frac{T_H}{(R_A+R_B)C}} = \frac{1.67}{3.33}$$

$$-\frac{T_H}{(R_A+R_B)C} \times \ln e = \ln(0.5)$$

$$+\frac{T_H}{(R_A+R_B)C} e = +\ln \frac{1}{0.5}$$

$$\frac{T_H}{(R_A+R_B)C} = 0.69$$

$$T_H = 0.69 (R_A+R_B)C.$$

T_L Calculation:

$$\frac{1}{3} V_{CC} = \cancel{\frac{0}{e}} + \left(\frac{2}{3} V_{CC} - \cancel{\frac{0}{e}} \right) e^{-\frac{T_L}{R_B C}}$$

$$\Rightarrow \frac{1}{3} \times 5 = \left(\frac{2}{3} \times 5 \right) \times e^{-\frac{T_L}{R_B C}}$$

$$\Rightarrow 1.67 = 3.33 \times e^{-\frac{T_L}{R_B C}}$$

$$\Rightarrow e^{-\frac{T_L}{R_B C}} = 0.5$$

$$\Rightarrow -\frac{T_L}{R_B C} = \ln 0.5$$

$$\Rightarrow \frac{T_L}{R_B C} = \ln \frac{1}{0.5}$$

$$\Rightarrow T_L = 0.69 R_B C.$$

Time period,

$$T = T_H + T_L$$

$$= 0.69 (R_A + 2R_B)C.$$

Frequency,


$$f = \frac{1}{T} = \frac{1}{0.69(R_A + 2R_B)C}$$

$$f = \frac{1.45}{(R_A + 2R_B)C}$$

Duty cycle,

$$D = \frac{T_H}{T} \times 100\%$$

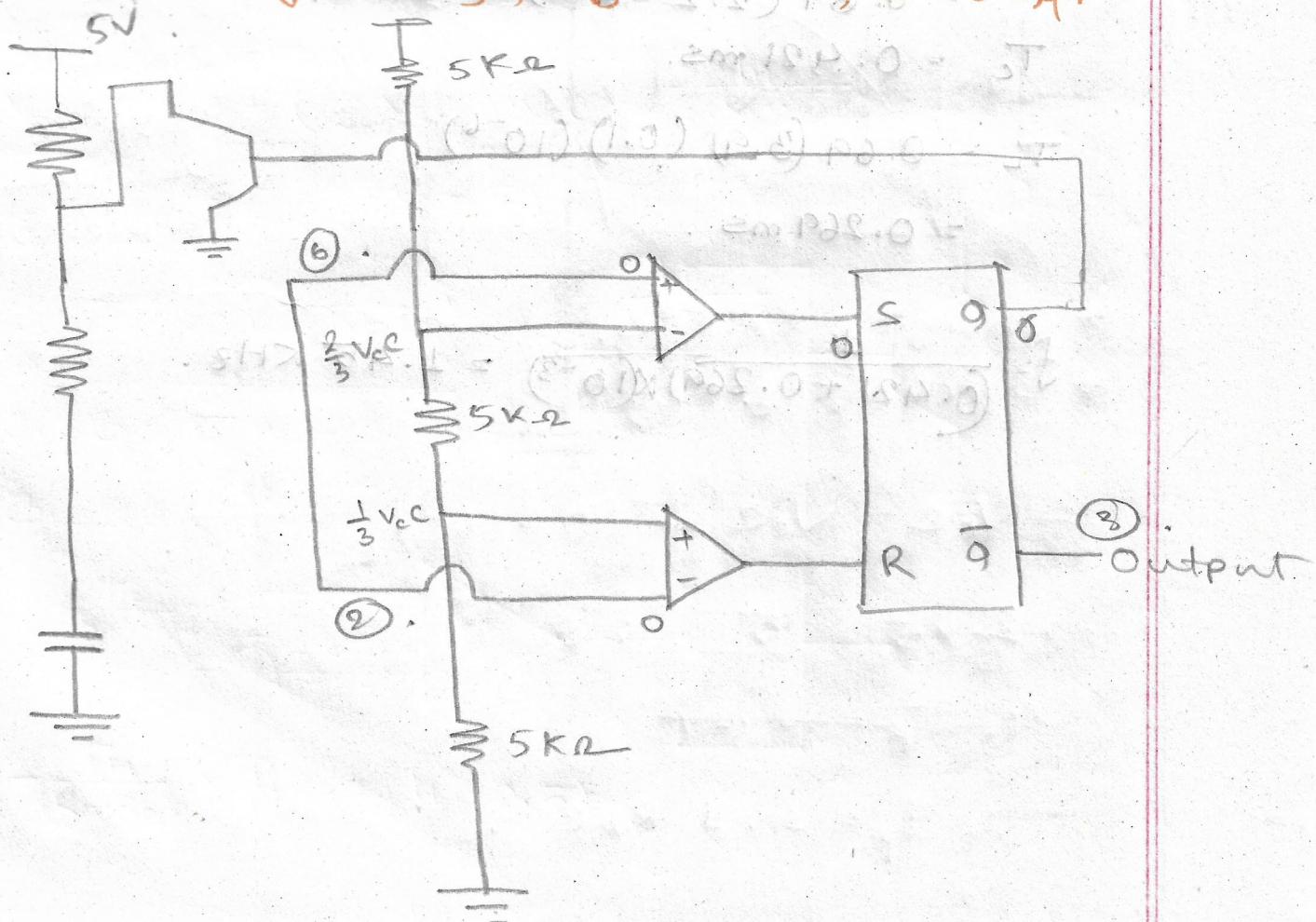Q Design a 3 stable Multivibrator circuit whose $f = 2\text{kHz}$, $R_B = 10\text{k}\Omega$, $C = 0.1\mu\text{F}$



$$T_H = (R_A + R_B)C \times 0.69.$$

$$\frac{1}{f} = T_H + T_L.$$

$$\Rightarrow \frac{1}{2 \times 10^3} = T_H \times (0.69 \times 10 \times 10^3 \times 0.1 \times 10^{-6})$$

8. In the astable multivibrator, $R_A = 2.2 \text{ k}\Omega$, $R_B = 3.9 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$. Determine the positive pulse width t_{12} , negative pulse width t_{21} and free running frequency.

$$T_H = 0.69(R_A + R_B)C$$

$$= 0.69(2.2 + 3.9) \times (0.1)(10^{-6}).$$


$$T_C = 0.421 \text{ ms.}$$

$$T_L = 0.69(3.9)(0.1)(10^{-6})$$

$$= 0.269 \text{ ms.}$$

$$f = \frac{1}{(0.421 + 0.269) \times 10^{-3}} = 1.45 \text{ kHz.}$$




Monostable Operation of 555 Timer.

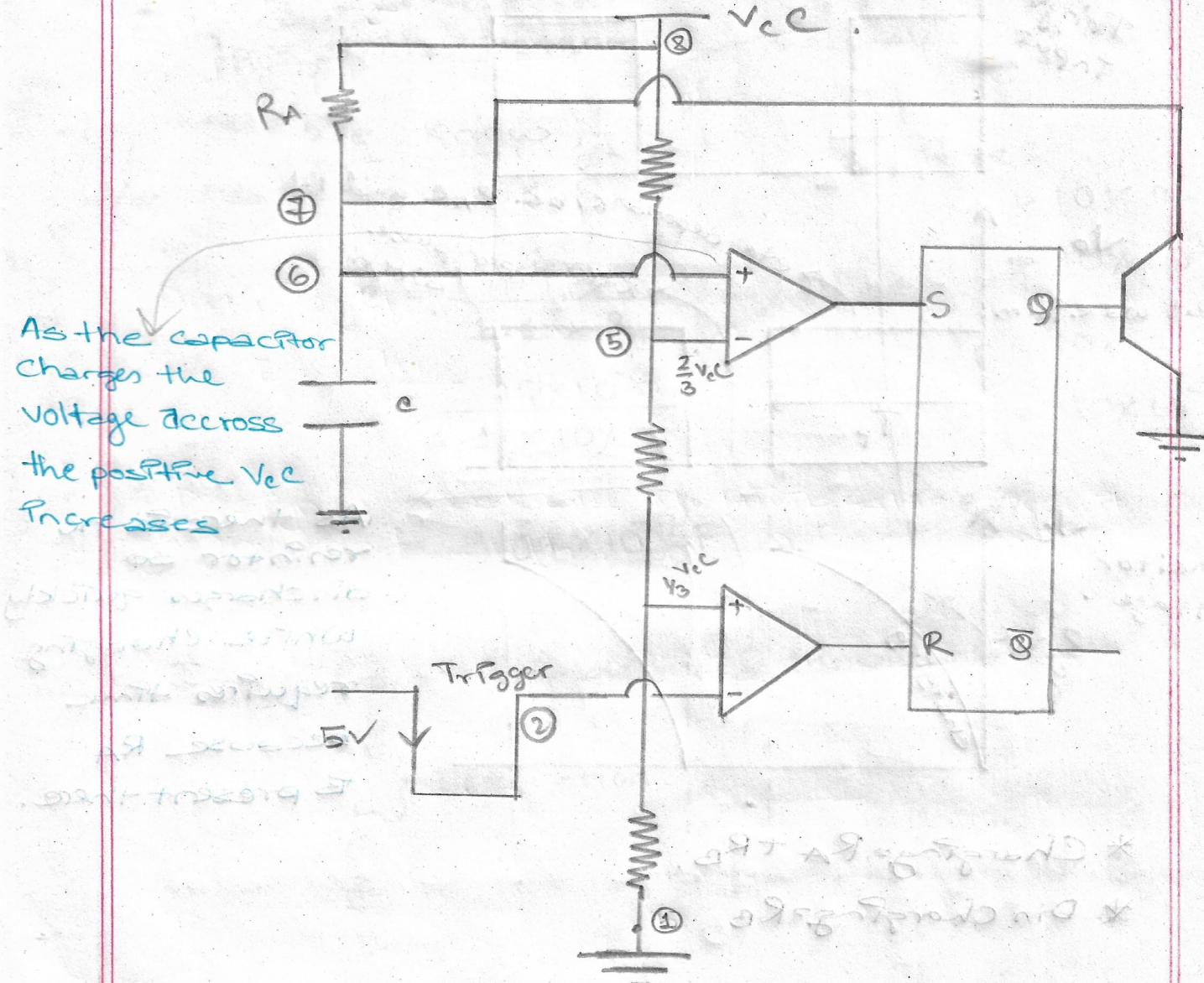

$$\frac{V_{CC}}{3} = 5(V - 0) + 5V = 5V \frac{1}{2}$$

$$5V \cdot \frac{1}{2} = T = 2 \times \frac{1}{2} C$$

$$5 \times R \cdot t = T$$

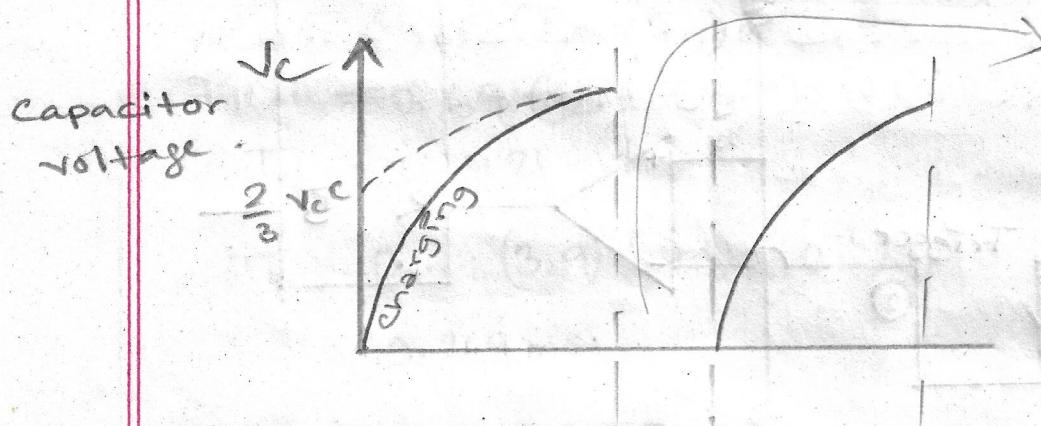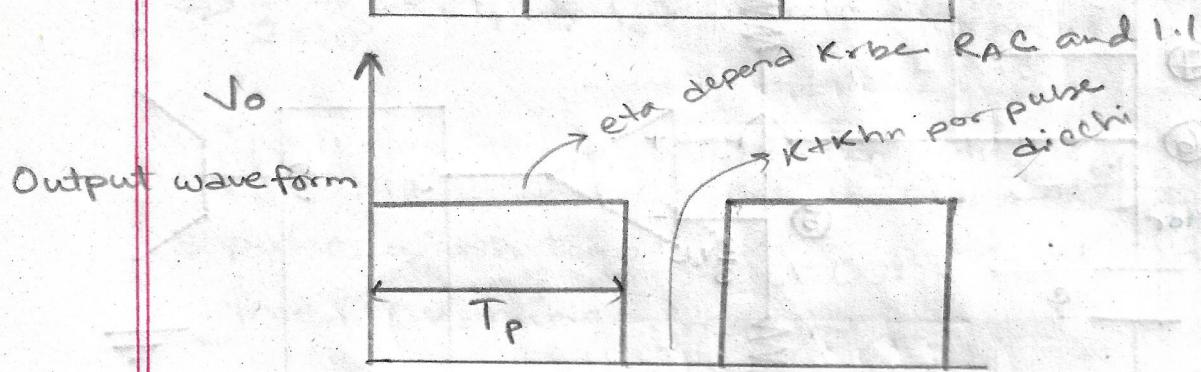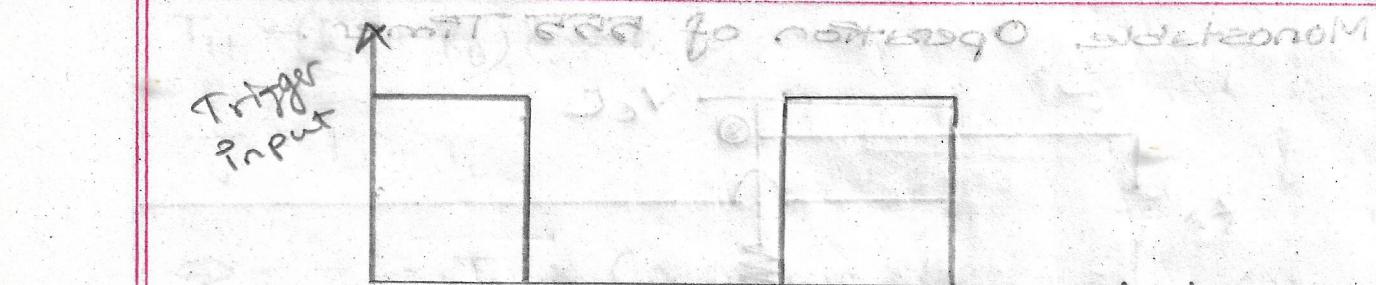

As there is no resistor so discharges quickly while charging requires time because R_A is present there.

* Charging = $R_A + R_B$

* Discharging = R_B

$$\frac{2}{3} V_{CC} = V_{CC} + (0 - V_{CC}) e^{-\frac{T_p}{R_{AC}}}$$

$$\Rightarrow \frac{2}{3} \times 5 = 5 - 5 e^{-\frac{T_p}{R_{AC}}}$$

$$\therefore T_p = 1.1 A$$

$$\therefore T_p = 1.1 R_{AC}$$

8. For a monostable operation of 555 Timer, their $R_A = 10\text{ k}\Omega$, the pulse width $T_p = 10\text{ ms}$. Determine the value of C .

We Know,

$$T_p = 1.1 R_A C.$$

$$C = \frac{T_p}{1.1 \times R_A}$$

$$= \frac{10 \times 10^{-3}}{1.1 \times 10 \times 10^3}$$

$$= 9.09 \times 10^{-7} \text{ F}$$

Here

$$R_A = 10\text{ k}\Omega$$

$$= 10 \times 10^3 \text{ }\Omega$$

$$T_p = 10\text{ ms.}$$

$$= 10 \times 10^{-3} \text{ s.}$$

$C = ?$

Imp: from astable and monostable

T_H
 T_L } Derivation.

C

F

Duty



$T_p \rightarrow$ Derivation.

Graphical representation.

Square wave generator using Op-Amp.

to be made
equation formed
as shown

equation to be

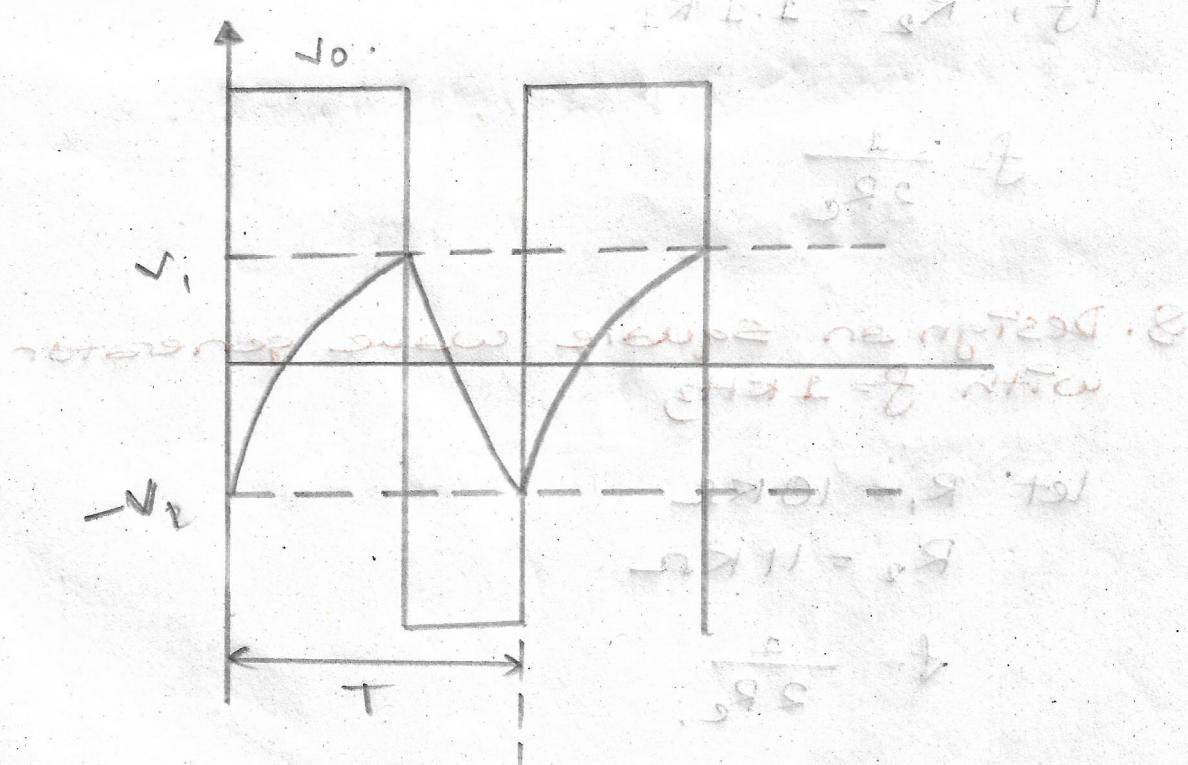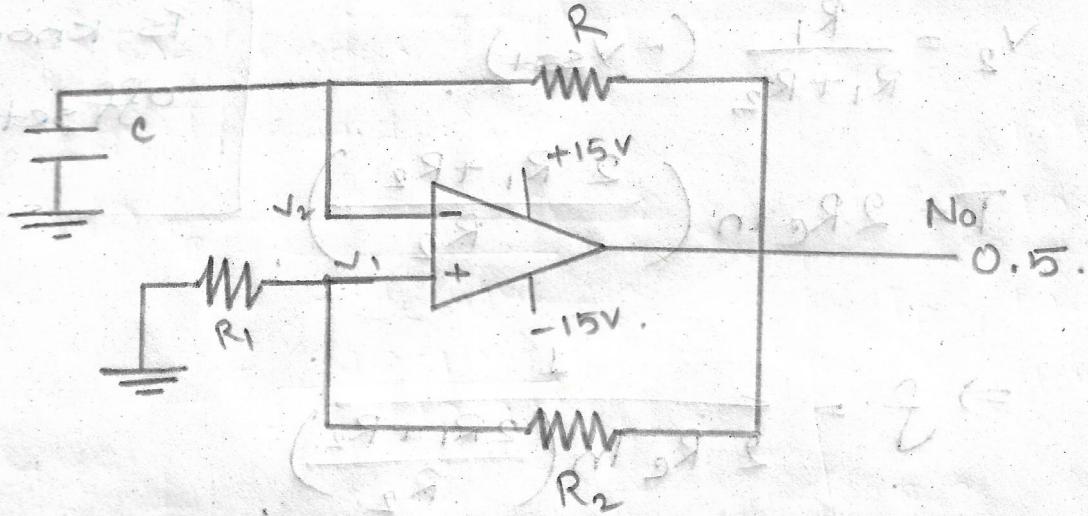

$$V_1 = \frac{R_1}{R_1 + R_2} (+V_{sat})$$

OR,

$$V_2 = \frac{R_1}{R_1 + R_2} (-V_{sat})$$

$$T = 2 R_c \ln \left(\frac{2 R_1 + R_2}{R_2} \right)$$

Note: When we get lowest voltage it is known as offset voltage.

$$\Rightarrow f = \frac{1}{2 R_c \ln \left(\frac{2 R_1 + R_2}{R_2} \right)}$$

$$Pf, R_2 = 1.1 R_1$$

$$f = \frac{1}{2 R_c}$$



8. Design an square wave generator with $f = 1 \text{ kHz}$

$$\text{let } R_1 = 10 \text{ k}\Omega$$

$$R_2 = 11 \text{ k}\Omega$$

$$f = \frac{1}{2 R_c}$$

Triangular wave generator

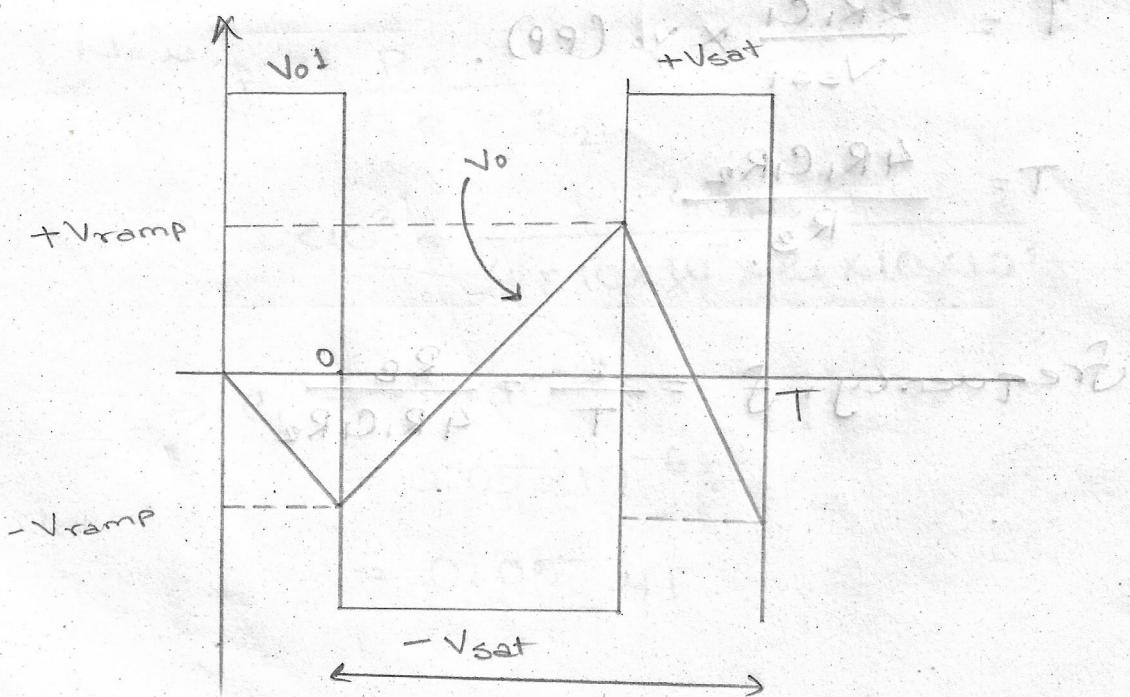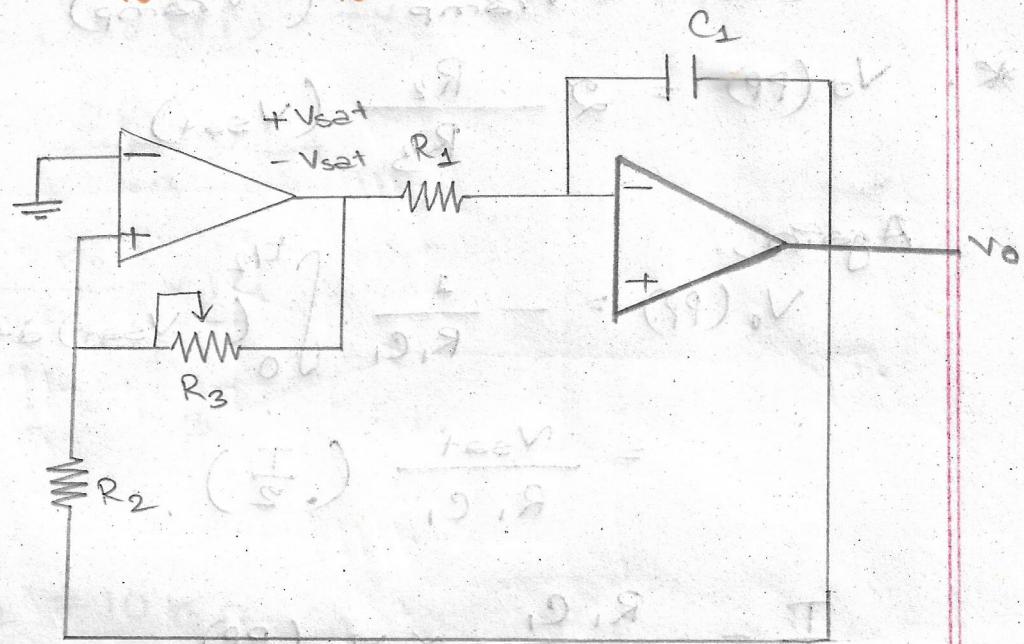

$$+V_{ramp} = -\frac{R_2}{R_3} (-V_{sat})$$

$$-V_{ramp} = -\frac{R_2}{R_3} (+V_{sat}).$$

$$V_o(PP) = +V_{ramp} - (-V_{ramp})$$

* $V_o(PP) = 2 \frac{R_2}{R_3} (V_{sat})$

Again,

$$V_o(PP) = -\frac{1}{R_1 C_1} \int_0^{T/2} (-V_{sat}) dt.$$

$$= \frac{V_{sat}}{R_1 C_1} \left(\frac{T}{2} \right).$$

$$\frac{T}{2} = \frac{R_1 C_1}{V_{sat}} \times V_o(PP).$$

$$T = \frac{2 R_1 C_1}{V_{sat}} \times V_o(PP).$$

$$T = \frac{4 R_1 C_1 R_2}{R_3}$$

$$\text{frequency, } f = \frac{1}{T} = \frac{R_B}{4 R_1 C_1 R_2}$$

$$(100V) \frac{dV}{dt} = 9mA V$$

$$(100V) \frac{dV}{dt} = 9mA V$$

Q. Design a triangular wave generator of
 $f = 2 \text{ kHz}$, $V_o (\text{PP}) = 7 \text{ V}$ $V_{\text{sat}} = 14 \text{ V}$.

$$V_o (\text{PP}) = \frac{2R_2}{R_3} V_{\text{sat}}$$

$$\Rightarrow 7 = \frac{2R_2}{R_3} \times 14$$

$$\Rightarrow 4R_2 = R_3$$

Let,

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 40 \text{ k}\Omega$$

$$\text{Now, } f = \frac{R_3}{4R_1 C_1 R_2}$$

$$\Rightarrow 2 \times 10^3 = \frac{40 \times 10^3}{4 \times 10 \times 10^3 \times C_1 \times 10 \times 10^3}$$

$$\Rightarrow C_1 = 5 \times 10^{-8} \text{ F}$$

$$= 0.05 \times 10^{-6} \text{ F}$$

$$= 0.05 \mu\text{F}$$